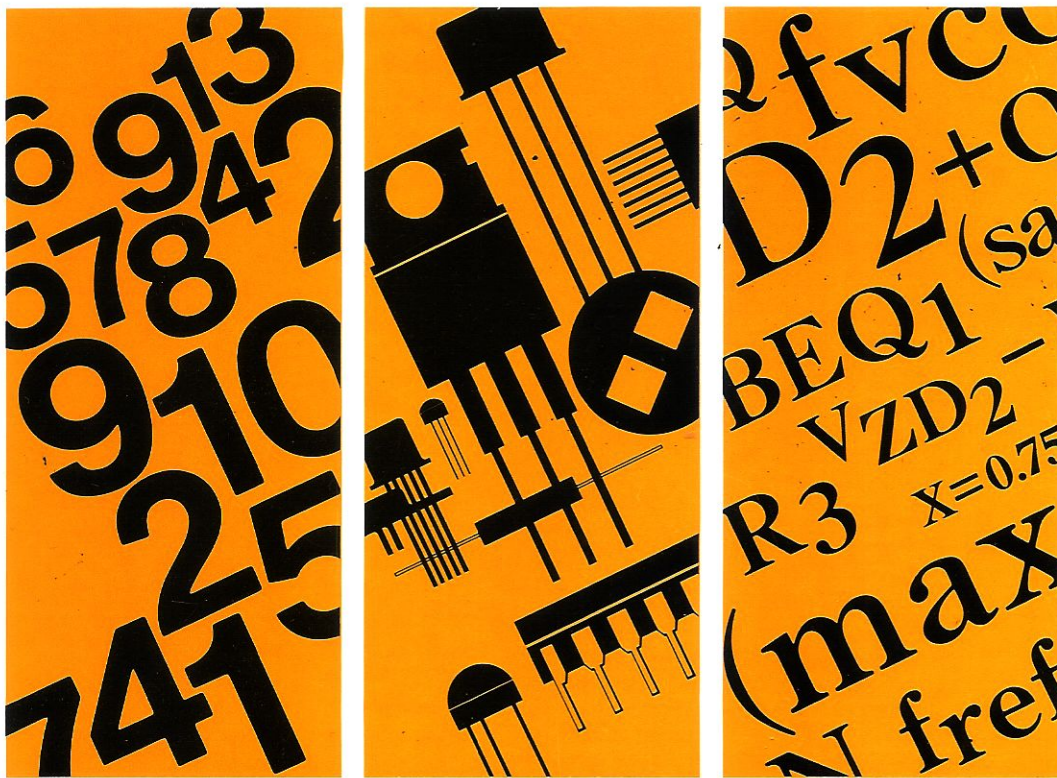




Contents

SECTION I – INDEX BY NUMBER	1
Application Briefs	2
Application Notes	4
Technical Papers	5
Systems Bulletins	5
 SECTION II – INDEX BY PRODUCT	 7
Transistors	8
Diodes	9
Electro-Optical Devices	9
Digital Integrated Circuits	8
Linear Integrated Circuits	9
MOS Circuits	9
Memory Circuits	9
Hybrid Circuits	9
Special Circuits	9
 SECTION III – INDEX BY FUNCTION	 11

**Index
By
Number**



APPLICATION BRIEF INDEX by Number

- AB — 4 Sliding Scale Power Supply, 1964
- 6 Printed Circuit Attachments for Cerpak™ Flat Package Construction Aids, 1965
- 7 The Micrologic* 914 Binary — Circuit Aids, 1965
- 8 Minimum Pulse Width Discriminator, 1965
- 9 Clock Circuits for Micrologic Systems, 1965
- 13 Numeric Character Generator Using Integrated Circuits, 1965
- 14 A Frequency Comparison Circuit, 1965
- 16 Dual-In-Line Breadboard for Integrated Circuits Construction Aids, 1966
- 18 Breadboard Unit for Integrated Circuits
- 19 Tape Reader and Display
- 21 Numeric Control X-Y Table Using Integrated Circuits
- 22 A Digital Clock
- 23 Bi-Directional Counters, 1968
- 24 Using the DTμL 945/948
- 25 Lead-Forming and Trimming Tool
- 27 Micrologic Integrated Circuit Amplifier
- 28 DTμL Power Dissipation
- 29 Power Supply Circuits, 1968
- 31 A Simple D/A or A/D Converter, 1967
- 32 Stepping Motor Translator, 1967
- 33 Synthesis of Nonconstant Weight Counters Using J-K Flip-Flops, 1967
- 34 Using a Standard Television Monitor as an Alpha-Numeric Display, 1967
- 35 Linear Applications of Digital Integrated Circuits, 1967
- 36 CμL 9960 Operation, 1967
- 37 Pulse Frequency Difference Generator, 1967
- 38 DTL Skew Time Measurement Tester, 1967
- 39 Instant Square Root Generation, 1967
- 40 DTL Function Tester, 1967
- 43 High-Speed Stepping Motors, 1967
- 44 Gated Pulse Rate Function Multiplier, 1967
- 45 Application of the μA716C as a Wien Bridge Oscillator, 1967
- 47 A TV Sync Generator Using Complex Function Integrated Circuits, 1967
- 48 Forward-Biased Second Breakdown, 1967
- 50 Multi-Signal Processing Circuit, 1967
- 51 Analog-to-Pulse Width Converter, 1968
- 52 Single FET Audio Oscillator, 1967
- 53 Signal Processing in Industrial Control Systems, 1968
- 54 Variable-Area, Four-Quadrant Analog Multiplier, 1968
- 55 Using the 9300 Four-Bit Shift Register to Generate Linear Pseudo-Random Sequences for Transmission Through Heavy Noise, 1968
- 56 Decade Programmable Divider Using the 9300, 1968
- 57 DTL One-Shots, 1968
- 58 A Complementary Power Amplifier Without Bias, 1968
- 59 Design of UHF TV Tuners Using Silicon Transistors, 1968
- 60 Revolutionary Power Supplies Using FET's, 1968
- 61 The MOS FET as a Low-Level Chopper, 1968
- 62 An Eight Bit D-to-A Using Only ICs, 1968
- 63 9935 Hex Inverter, 1968
- 66 FM Stereo Multiplex Decoder, 1968
- 68 A Chokeless, Vertical-Deflection Circuit for Small-Screen, Black-and-White Sets, 1968
- 69 A Locked Oscillator for Color TV Using an FET as the Control Element, 1968
- 70 Operation of Avalanche Luminescent Diode Array, 1968
- 71 Medium-Power Silicon Transistor DC-to-DC Converters, 1968
- 72 Design Concepts for Low-Cost, Low-Power, Audio Amplifier Transistors, 1968
- 73 Precision Random Event Scaler, 1969
- 74 A Hybrid Color TV Review, 1968
- 76 An MSI Approach to Multiplexing Mode Operation of a Low-Voltage Vacuum Tube 7-Segment Numeric Display, 1969

*Registered trademark of Fairchild Camera and Instrument Corporation

77	Solid State TV Signal Distribution, 1968
79	A 100-Watt Solid State Inverter, 1968
80	A Color TV Video IF Amplifier with a Novel AGC Circuit, 1968
81	A Hot Electron Diode for Video Detectors and UHF Mixers, 1968
82	High-Performance Phonograph Preamplifier Utilizing the 2N5138 and the SE4021, 1968
84	CRT Deflection Amplifier for Numeric Displays, 1968
85	Some Useful Signal-Processing Circuits Using FET's and Operational Amplifiers, 1968
86	Some Characteristics of Junction FET's in the Linear Region, 1968
88	An All-Solid-State Electronic Imaging Device in a Facsimile Reproduction Application, 1969
91	An Economical D/A or Staircase Generator Using the μ A739, 1969
93	I/O Typewriter/ASC11 Code Converter, 1969
95	A High-Quality Video IF for Color TV, 1969
96	Design Considerations for an Optical Tape Reader Using a Plastic Phototransistor, 1969
97	Multi-Port Memory Using MSI, 1969
99	μ A733 Oscillators, 1969
100	A Light Sensitive Logic Gate and its Applications, 1969
101	Logic Control of Mechanical Systems Made Easy with MSI, 1969
102	Vidicon Head Amplifiers, 1969
103	A Signal-Processing Circuit for a Black-and-White TV Camera, 1969
104	Black Level Considerations in High-Quality TV Receivers, 1969
105	Uses and Abuses of the Chroma Demodulator, 1969
106	Applications of the SE5030, 1969
107	Utilizing Bimesar TM Complementary Power Transistors in Class A Driven Power Amplifiers, 1969
108	15-W and 30-W Complementary Amplifiers Featuring Bimesar Power Transistors, 1969
109	A 50W Class A Driven Amplifier Featuring the PFB2802 and PFB4802, 1969
110	A 70-W Class A Driven Complementary Amplifier Featuring the PFB 2902 and PFB 4902, 1969
111	A High Speed, Zero Input Current Chopper Amplifier, 1969
112	A Frost Sensor for Home Refrigerators
113	Power Gain as a Design Criterion for Thyristor Temperature Controllers
114	A New Gate Drive System for Bidirectional SCR Circuits, 1969
115	A Unidirectional Regenerative Triggering System, 1969
116	Combination Timer and Speed Control
117	Heat Sinks for Epoxy Transistors
118	Novel Distributional Data for a New IF Amplifier Transistor with Faraday Shielding
119	A High Speed Differential Preamplifier for Thin Film Memories, 1969
121	The μ A715 — A Versatile High Speed Operational Amplifier, 1969
122	A Monolithic Radiation-Resistant Operational Amplifier, 1969
123	A Micropower Monolithic Operational Amplifier, 1969
124	The μ A746E Color TV Chroma Demodulator IC, 1969
125	Applications of the μ A749 Dual Operational Amplifier, 1969
126	The μ A749 Dual Operational Amplifier, 1969
127	A Trapezoidal Deflection Circuit for Use with the 3250 Numeric Character Generator Using the μ A715, 1969
128	A High Speed Sample and Hold Using the μ A715, 1969
129	Low-Pass Active Filter for Electronic Imaging Using the μ A715, 1969
130	μ A725 AGC Amplifier, 1969
131	An Arithmetic Analog Computer Using μ A735 Logarithmic Amplifiers, 1969
132	Active Filters with Gain Using the μ A725, 1969
133	More Voltage Regulator Applications Using the μ A723, 1969
134	The Frequency Division Multiplex Channel Amplifier with the μ A748, 1969
136	A Low-Drift, Low-Noise Monolithic Operational Amplifier for Low Level Signal Processing, 1969
139	Serial Numeric Display System, 1970
140	Partitioning Logic System for 3400 Micromosaic TM , 1970
141	The 9300 as a 2-Input Shift Register, 1970
142	Generating the Square of a Binary Number, 1970
143	TV Intermediate Frequency Modulator, 1970
144	A Minimum Component μ A749 Voltage-to-Frequency Converter with 1% Accuracy, 1970
145	Cost Savings with Custom MSI Designs, 1970
146	Even More Voltage Regulator Applications Using the μ A723 — Number 2, 1970

APPLICATION NOTE INDEX by Number

- APP — 41/2 Stable Wideband Emitter Followers, 1962
- 59 An Improved Emitter-Coupled Multivibrator, 1963
- 61/2 Long-Delay Transistor Timer, 1967
- 67 Video Amplifier Design for Transistor TV Receivers, 1967
- 87/1 A Varactor Bias Servo System, 1965
- 93 Transient Response Characteristics of Phototransistors, 1966
- 103 Applications of the Silicon Planar Field-Effect Transistor, 1964
- 105/4 A Monolithic Operational Amplifier, 1966
- 107 Diode Transistor Micrologic*, 1967
- 111/3 The Improved μ A702 Wideband DC Amplifier, 1965
- 112 The Measurement of Transistor Small Y Parameters, 1965
- 114 μ A702 Circuit Design Ideas, 1966
- 116 The Operation and Use of a Fast Integrated Circuit Comparator, 1966
- 117/2 Frequency-Compensation Techniques for an Integrated Operational Amplifier, 1966
- 123 Core Memory Sense Amplifier Designs Using an Integrated Circuit, 1966
- 124 Designing with Off-the-Shelf Linear Microcircuits, 1966
- 125 A Versatile Tester for Linear Integrated Circuits, 1966
- 128 Complementary Transistor Micrologic Integrated Circuits, 1967
- 130 Aids for Digital IC Systems, 1967
- 131 Transistor-Transistor Micrologic Integrated Circuits, 1967
- 135 Performance of the μ A703 in 100MHz and 200MHz Amplifiers and 100MHz Harmonic Mixers, 1967
- 136 A Simple Current-Limited Regulated Laboratory Power Supply, 1967
- 137 Four-Transistor Line-Operated AM Radio, 1967
- 141 Transistorized TV Horizontal Driver System, 1967
- 143 A Horizontal Oscillator for Transistorized TV Set, 1967
- 144 Frequency Synthesizer for 27-MHz Citizens' Band Transceiver, 1967
- 145 Color Television Chroma Reference Systems Using the μ A703, 1967
- 146 Color TV Sound System Using the Fairchild μ A703, 1967
- 147 Characterization and Application of the μ A703 in Four-Stage, High-Quality FM-IF Amplifier, 1967
- 149 Semiconductor Circuits for 19-Inch Black-and-White Television Receivers, 1967
- 150 Semiconductor Circuits for Hybrid Color Television, 1967
- 151 High-Performance Integrated FM-IF Strips, 1967
- 152 250-MHz Distributed Amplifier Suitable for CATV Trunk Line, 1967
- 153 Logic Designs Using the T μ L9008, 1967
- 154 Compatible Current Sinking Logic, 1967
- 155 Industrial Code Conversion, 1967
- 156 Designing with the μ A703 Monolithic RF-IF Amplifier, 1967
- 157 A Fixed-Gain Low-Distortion AF Amplifier, 1967
- 158 Two High-Performance Monolithic Microcircuits for FM Sound System, 1968
- 159 A Low-Cost AM-FM Radio Employing an Integrated Circuit Design, 1967
- 160 Applications of the CCSL 9301 Decoder, 1967
- 161 CCSL 9300 Shift Register, 1967
- 163 Applications of the CCSL 9304 Dual Adder, 1967
- 164 Application of the μ A722 10-Bit Current Source, 1968
- 165 SH-3200, SH-3201 Hybrid DC Voltage Regulator, 1968
- 166 HLLD T μ L High-Noise-Immunity Integrated Circuits, 1968
- 167 MSI 9308 Dual 4-Bit Latch, 1968
- 168 Applications of the 9034 Read-Only Memory, 1969
- 169 CCSL 9306 Up/Down Counter, 1969
- 170 Applications of the 9311 1-out-of-16 Decoder, 1969
- 171 Applications of the μ A739 and μ A749 Dual Preamplifier Integrated Circuits in Home Entertainment Equipment, 1969
- 172 The 3800 Arithmetic Unit, 1969
- 173 The 9601, A Second Generation Retriggerable One-Shot, 1969
- 174 A Low-Cost Hybrid Color TV Receiver, 1969
- 175 The μ A739, A Low-Noise Dual Operational Amplifier, 1969
- 176 An Avionics Digital Frequency Synthesizer, 1969
- 177 The Hot Carrier Diode, 1969
- 178 A Navigation Receiver that Uses a Digital Frequency Synthesizer, 1969

*Registered trademark of Fairchild Camera and Instrument Corporation.

- 179 Line-Operated Phono Circuits Using the PFB1400, 1969
- 180 A Low-Noise Tape Preamplifier, 1969
- 181 The 9309 and 9312 Multiplexers, 1969
- 182 The MSI 9328 Dual 8-Bit Shift Register, 1969
- 183 System Design Combining MOS and Bipolar Circuits, 1969
- 184 The 9310/9316 Counters, 1970
- 185 A New Silicon Transistor for UHF Application, 1970


TECHNICAL PAPER INDEX by Number

- TP – 27 Forward AGC Design Considerations in Transistorized Television Receivers, 1964
- 28 Measurement of Transistor High-Frequency Current Gain, 1964
- 32 A Unique Circuit Design for a High-Performance Operational Amplifier Especially Suited to Monolithic Construction, 1965
- 33 Some Circuit Design Techniques for Linear Integrated Circuits
- 35 A Black-and-White and Color TV Video IF Output Transistor, 1965
- 36 A Low-Noise AGC Silicon Transistor Useful from LF to UHF, 1967
- 37 Integrated Circuits in Industrial Control, 1967
- 38 Semiconductor Video Amplifiers for Monochrome and Color TV Receivers, 1966
- 39 A New 400-Volt Horizontal Output Transistor, 1966
- 40 Radiation Testing of Linear Microcircuits, 1966
- 41 Space and Nuclear Environments and their Effects on Semiconductors, 1967
- 42 Novel Multi-Purpose LIC's Introduce New Concepts into Circuit Design, 1967
- 43 Color TV Processing Using Integrated Circuits, 1967
- 44 Let's Clarify IC Noise Margins, 1967
- 46 TT μ L Integrated Circuits: High Speed Considerations, 1968
- 47 Design Concepts for Low-Cost Transistor AGC Systems, 1968
- 48 A Monolithic Chroma Demodulator Integrated Circuit for Color Television Receivers, 1968
- 50 A Small, Low-Cost, Hybrid Black-and-White Television Set, 1968
- 51 Proposed Integrated Circuit for Appliance or Process Control, 1969
- 52 TV Receiver Tuning Systems of the Future, 1969
- 53 A Digital Frequency Synthesizer for an AM and FM Receiver, 1969
- 54 Philosophy and Design of MSI, 1970

SYSTEMS BULLETIN INDEX by Number

- SB – 1 Semiconductor Devices in Military Communications Systems, 1969
- 2 Community Antenna Television, 1969
- 3 Closed Circuit Television, 1969
- 4 Television Receivers, 1970

Index By Product

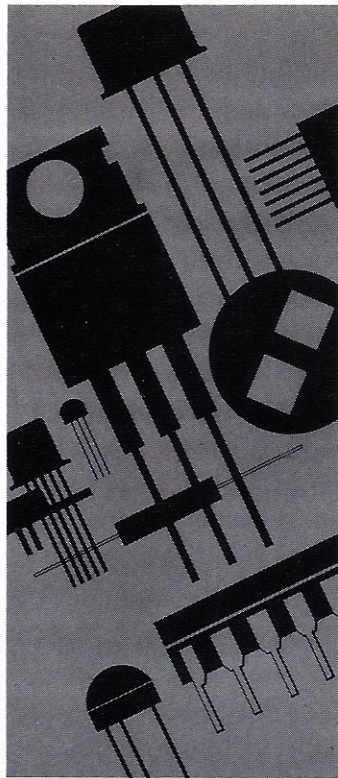


PRODUCT CATEGORY	APPLICATIONS BRIEFS	APPLICATIONS NOTES	TECHNICAL PAPERS
TRANSISTORS			
Switching	95	59	
General Purpose Amplifier	4, 52, 58, 60, 68, 72, 74, 77, 80, 82, 102, 103, 106, 107, 108, 109, 110	137, 141, 143, 149, 150, 174, 178, 180, 183	38, 47, 50
RF/IF Amplifier and Oscillator	48, 59, 74, 77, 80, 102, 106	61/2, 137, 144, 149, 150, 152, 174, 176, 178, 179	27, 35, 38, 43, 47, 50
Power	71, 79	179	
DIGITAL INTEGRATED CIRCUITS			
RT μ L Micrologic* ICs	7, 8, 9, 14, 19, 21, 22, 27, 35, 39, 73, 100	144	
LPRT μ L Low Power Micrologic ICs	22	154	
DT μ L Diode Transistor Micrologic	18, 24, 28, 32, 37, 38, 40, 43, 57, 63, 73, 100 145	107, 154, 166, 183	
TT μ L Transistor Transistor Micrologic	55, 73, 88, 101, 111, 139, 142, 143, 145	131, 153, 154, 160, 161, 163, 167, 169, 170, 173, 181, 182	44, 46, 53
MSI Medium Scale Integration	47, 55, 56, 76, 88, 93, 97, 101, 129, 139, 141, 142, 145	160, 161, 163, 167, 169, 170, 176, 181, 182, 184	53

*Registered trademark of Fairchild Camera and Instrument Corporation

PRODUCT CATEGORY	APPLICATIONS BRIEFS	APPLICATIONS NOTES	TECHNICAL PAPERS
DIODES			
Computer		61/2	
General Purpose		61/2	
Zener		179	
Hot Carrier		177	
ELECTRO - OPTICAL DEVICES			
Light Sensors	19, 37, 100	93	
Light Emitters	70		
Special Photo Products	96		
LINEAR INTEGRATED CIRCUITS			
	29, 43, 44, 45, 50, 51, 53, 54, 66, 74, 85, 91, 99, 102, 104, 105, 111, 119, 121, 122, 123, 124, 125, 126, 127, 128, 129, 130, 131, 132, 133, 134 136, 138, 143, 144, 146	105/4, 111/3, 114, 116, 117/2, 123, 124, 125, 135, 145, 146, 147, 149, 150, 151, 156, 157, 158, 159, 164, 171, 179, 180, 183,	32, 33, 40, 42, 43, 48
MOS CIRCUITS		172, 183	
MEMORY CIRCUITS		168, 170	
HYBRID CIRCUITS		165	
SPECIAL CIRCUITS			
C μ L Counting Micrologic* ICs	22, 36		
CT μ L Complimentary Transistor Micrologic	39	128, 144	

*Registered trademark of Fairchild Camera and Instrument Corporation

Index By Function

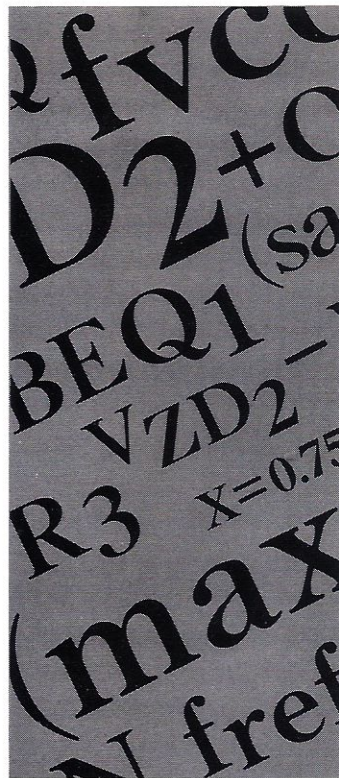

A

A-D CONVERTERS — See CONVERTERS.

ADDERS, DIGITAL — APP-107, APP-128, APP-131, APP-153, APP-154, APP-163, APP-172, APP-181

AFC (AUTOMATIC FREQUENCY CONTROL) — See AMPLIFIERS, AFC

ALARMS & ALARM SYSTEMS — AB-100, APP-114

AMPLIFIERS

AFC — APP-149, TP-50

AGC — AB-80, AB-85, AB-86, AB-130, APP-74, APP-151, APP-164, TP-50

Audio — AB-82, APP-103, APP-149, APP-158, APP-159, APP-171, APP-175, APP-179, TP-50

Bridge — AB-138

Buffer — APP-164

CATV — SB-2

Chopper — AB-61, AB-111

Comparator — AB-125, APP-116, APP-123

Compensation — AB-122, APP-117/2

Compressor — AB-86

DC — AB-126, APP-105/4, APP-111/3

Deflection — AB-68, APP-149, TP-39

Differential — AB-119

Distributed — APP-152

Driver — AB-70, AB-94, APP-141

Head (Vidicon Pre-Amplifiers) — AB-102

High-Frequency — TP-28

High-Fidelity — See AMPLIFIERS, Audio; AMPLIFIERS, Power

High Input Impedance — AB-121, APP-103

IF — AB-80, AB-95, AB-106, AB-118, APP-112, APP-121, APP-147, APP-149, APP-150, APP-151, APP-156, APP-158, APP-159, TP-50

Infrared — See SENSORS

Integrating — APP-105/4

Limiting — APP-111/3, APP-135, APP-147, APP-151, APP-158, APP-159

Linear — APP-105/4

Line-Operated — APP-179

Logarithmic — AB-131, APP-105/4, APP-124

Low-Noise — AB-136, APP-175, APP-180

Memory Sense — See AMPLIFIERS, Sense

Microwave — APP-185

Null — APP-105/4

Operational — AB-121, AB-122, AB-123, AB-125, AB-126, AB-127, AB-128, AB-136, APP-105/4, APP-111/3, APP-117/2, TP-32

Phono — AB-82, APP-179

Photo — AB-138

Power — See also THYRISTER — APP-116

Power-Audio — AB-58, AB-72, AB-94, AB-107, AB-108, AB-109, AB-110, AB-112, AB-113, AB-114, AB-115, APP-142, APP-175, APP-179

Preamp — AB-82, AB-85, AB-119, APP-123, APP-171, APP-175, APP-180

Public Address — See AMPLIFIERS, Audio

Pulse — APP-41/2

Radiation Resistant — AB-122

RF — AB-118, APP-112, APP-135, APP-156, TP-28

Sample-and-Hold — AB-128

Sense — AB-113, APP-123

Sensor — AB-113, AB-138, APP-105/4

Servo — APP-124

AMPLIFIERS — (Continued)

Strain Gauge — See AMPLIFIERS, Sensor

Sweep — See AMPLIFIERS, Deflection

Telemetry — AB-123

Thermocouple — See AMPLIFIERS, Sensor

Transducer — See AMPLIFIERS, Sensor

Unity Gain — APP-103

Vibration Pickup — See AMPLIFIERS, Sensor

Video — AB-99, AB-106, AB-119, AB-121, APP-67, APP-149, APP-150, TP-50

Wideband — AB-118, AB-119, AB-121, APP-41/2, APP-111/3, APP-152

AM RADIO — See COMMUNICATIONS SYSTEMS, Broadcast

ANALOG COMPUTERS — See COMPUTERS, Analog

APPLIANCE — See THYRISTER

ARITHMETIC LOGIC UNITS — AB-39, AB-142, APP-163, APP-167, APP-172, APP-181, APP-182, TP-54

AVIONICS — See COMMUNICATION SYSTEMS, INSTRUMENTATION

B

BOARDS — PRINTED CIRCUIT — See PACKAGING SYSTEMS

BRIDGES — APP-105/4

C

CALCULATORS — See COMPUTERS, DESK TOP

CATV SYSTEMS & EQUIPMENT — See COMMUNICATION SYSTEMS

CCTV SYSTEMS & EQUIPMENT — See COMMUNICATION SYSTEMS

CHOPPERS — AB-61, APP-103

CITIZENS' BAND — See COMMUNICATION SYSTEMS

CLAMPERS — APP-105/4

CODE CONVERSION — AB-93, AB-101, APP-155, APP-163

CODES — APP-164

CODERS — See DECODERS, ENCODERS

COLOR TELEVISION — See TELEVISION

COMMUNICATION SYSTEMS

Avionics — APP-176, APP-178

Broadcast

AM Radio — APP-137, APP-151, APP-159, TP-53

FM Radio — APP-135, APP-147, APP-151, APP-158, APP-159, TP-53

CATV (Community Antenna Television) — SB-2

CCTV (Closed Circuit Television) — AB-102, AB-103, SB-3

Citizens' Band — APP-144

Data — AB-55

Facsimile — APP-114

Military — SB-1

Pulse Modulation

PAM — AB-50

PDM — AB-50, AB-51, APP-173

Synthesizers — APP-144, APP-176, APP-178, TP-52, TP-53

Telemetry — APP-114

Telephone — AB-134, APP-114

Transceivers — APP-144

COMPARATORS, ANALOG — APP-116, APP-123, APP-124

COMPARATORS, DIGITAL

Binary Magnitude — APP-153, APP-163, APP-181

Frequency — AB-14

Frequency/Phase — AB-14, APP-176

Phase — APP-176

COMPRESSORS, DATA & SPEECH — AB-85

COMPUTER

Logic Circuits — TP-44, TP-46

COMPUTERS

Analog — AB-131

COMPUTING EQUIPMENT, PERIPHERAL — See CONVERTERS, COUNTERS, PRINTERS, etc.

CONTROLS

Digital — AB-23, AB-33, AB-43, AB-63, AB-100, AB-101, APP-166, TP-37

Motor — APP-172

Numeric — TP-37

Process — TP-51

Proportional — TP-51

Remote — APP-171, TP-51

Sequential — TP-51

Temperature — AB-113

CONVERTERS

Analog-to-Digital — AB-128, APP-164, APP-169, APP-170

Analog-to-Pulse — AB-51

Binary-to-Decimal — APP-160, APP-170

Binary-to-Gray — APP-131

Code — AB-93, APP-155, APP-163

DC-to-AC — AB-30, AB-71

Digital-to-Analog — AB-62, AB-91, APP-164, APP-172, APP-184

Accuracy & Speed — APP-164

Logarithmic — APP-164

Facsimile — AB-88

Frequency-to-Voltage — AB-35, AB-50

Frequency — See MIXERS

Gray-to-Binary — APP-163

Keyboard-to-Binary — APP-181

Parallel-to-Serial — APP-161, APP-181

Power Frequency — TP-51

Pulse-to-Analog — AB-50, TP-51

Resistance-to-Frequency — APP-173

Serial-to-Parallel — APP-161

UHF-to-VHF — AB-59

Voltage-to-Frequency — AB-144, APP-124, APP-173

"X"-to-ASCII — AB-93

COUNTERS — AB-32

BCD — AB-23, APP-120/2, APP-131, APP-169, APP-184

Binary — AB-23, AB-33, APP-128, APP-131, APP-154, APP-172, APP-184

Bi-Quinary — AB-23

Decade — APP-107, APP-128, APP-131, APP-160, APP-161, APP-184

Decimal — APP-128

Programmable — AB-56, APP-144, APP-160, APP-161, APP-169, APP-170, APP-176, APP-184, TP-53

Random — AB-73, APP-182

Shift — AB-23, AB-56, APP-85/3, APP-107, APP-128, APP-161, APP-176, APP-182

Up-Down — AB-23, APP-107, APP-131, APP-160, APP-161, APP-169, APP-184

CRYSTALS, SEMICONDUCTOR

HED — APP-177

CURRENT SENSORS — See SENSORS

CURRENT SOURCES — APP-164, APP-165

Integrated Circuit Design — APP-164

D

DATA

Acquisition & Reduction Systems — APP-153

Transmission Systems — AB-55

DECODERS

Binary-to-Decimal — See also CONVERTERS — APP-160

Color Television — See TELEVISION

Digital — AB-26, APP-160, APP-170

Digital-to-Analog — See CONVERTERS

DEMODULATORS

Color TV — See TELEVISION

Digital — APP-169, APP-173

FM — APP-158, APP-159

Phase — AB-14

Pulse — APP-172

DEMULTIPLEXERS, DIGITAL — AB-63, APP-160, APP-170

DETECTORS — See also DEMODULATORS

Digital — APP-173

Level — AB-100, AB-112, AB-113, AB-116, APP-114, APP-116, APP-124, TP-51

Limit — See DETECTORS, Level

Peak, Peak-to-Peak — APP-105/4, APP-124

Phase — AB-8, APP-105/4, APP-144, APP-158, APP-159, APP-176

Threshold — See DETECTORS, Level

Zero-Crossing — See also DETECTORS, Level — APP-114

DIFFERENTIATOR — See AMPLIFIER

DIGITAL

Analyzers — See ANALYZERS, DIGITAL

Comparators — See COMPARATORS, DIGITAL

Computers — See COMPUTERS, DIGITAL

Decoders — See DECODERS, DIGITAL

Demultiplexers — See DEMULTIPLEXERS, DIGITAL

Encoders — See ENCODERS, DIGITAL

Filters — See FILTERS, DIGITAL

Multiplexers — See MULTIPLEXERS, DIGITAL

Programmings — See CONTROLS, DIGITAL

Timing — AB-63

DISCRIMINATORS, PHASE — See DETECTORS, Phase

DISCRIMINATORS, SOUND — See DEMODULATORS

DISPLAYS

Character Generation — APP-168

CRT — AB-84, APP-76, APP-114, APP-168

Incandescent — AB-101, APP-166

Numeric — AB-36, AB-76, AB-84, AB-139, APP-182, TP-54

TV — See DISPLAYS, Raster Scan.

DIVIDER — See COUNTERS

DIVISION — APP-172

E

ENCODERS — See also DECODERS

Binary — APP-155, APP-170

Codes — APP-155

Color Television — See TELEVISION

Digital — APP-163

Error-Correcting — APP-163

Error-Detecting — APP-163

F

FACSIMILE — See COMMUNICATION SYSTEMS, CONVERTERS, IMAGING DEVICES

FILTERS, ANALOG

Active — AB-85, AB-129, AB-132

Low-Pass — AB-129

Tuneable — AB-85

FLIP-FLOPS — See MULTIVIBRATORS, Bistable

FM RADIO — See COMMUNICATION SYSTEMS, Broadcast; AMPLIFIERS

FREQUENCY SYNTHESIZERS — See SYNTHESIZERS, FREQUENCY

FUNCTION GENERATORS — See also AMPLIFIERS

Analog — AB-39, APP-164, APP-172

Digital — APP-160, APP-181

G

GATES, COMPUTER CIRCUIT — See CIRCUITS, Integrated; MODULES, Logic
GENERATORS

Analog — See POWER SUPPLIES; CONVERTERS, Digital-to-Analog

Clock — APP-163

Numeric Character — AB-13, AB-127

Pattern — APP-181

Pulse — AB-100, APP-173

Random Number — APP-182

Staircase — AB-91, APP-172

Sweep — See AMPLIFIERS, Deflection — APP-77, APP-114

Time Delay — AB-8, AB-57, APP-166

Timing, Digital — AB-57

TV Synch — AB-47

GUIDANCE SYSTEMS — See NAVIGATION SYSTEMS

H

HEAT SINKS — See PACKAGING

HIGH FIDELITY

FM Multiplex — AB-66

Tape Recorders — APP-180

HYBRID CIRCUITS — See CIRCUITS, Hybrid

IMAGING DEVICES — AB-88, AB-129

INDICATORS — See DISPLAYS

INSTRUMENTATION

Communication — See COMMUNICATION SYSTEMS

Control — See CONTROLS

Digital — See COUNTERS; SCALERS

Environmental — TP-51

Nuclear — AB-73, APP-114

Process — AB-37

Test Equipment — APP-112

Tester/Second Breakdown — AB-48

INTEGRATED CIRCUITS — See CIRCUITS, Integrated

INTEGRATORS

Analog — See AMPLIFIERS

Digital — APP-169

INTERFACE OF LOGIC ELEMENTS — APP-164, APP-166, APP-183

INVERTERS — See CONVERTERS; LOGIC, Circuits; POWER SUPPLIES

K

KEYING; FREQUENCY SHIFT — See COMMUNICATION SYSTEMS

L

LAMP DRIVERS — See also AMPLIFIERS — APP-166

LEVEL DETECTORS — See DETECTORS, Level

LIGHT AMPLIFIERS — See AMPLIFIERS

LIMIT DETECTORS — See DETECTORS, Level

LIMIT DIGITAL — See COMPUTER, Digital

LINE RECEIVERS — APP-116

LOGIC

Analysis — APP-154

Design — APP-154, APP-181

Elements — AB-24, AB-63

Interface — TP-44, TP-46

Partitioning — AB-140

Simulation — Fairsim Manual

LSI

"Plan Ahead for LSI"

"An LSI Approach Micromatrix "

"4500 Micromatrix Array Design HBIC"

"T²L Micromatrix Arrays"

"4600/4700 Micromatrix Array Design HBIC"

M

MAGNETIC TAPE RECORDERS — See also RECORDERS

MATRICES, COMPUTER — See BOARDS, Programming

MEMORIES

 Last-In-First-Out (LIFO) — APP-169

 Magnetic Thin Film

 Core — APP-123

 Multiple Address — AB-97, APP-181

 Read-Only — APP-168

 Semiconductor MOS — AB-97

 Bi-polar — AB-97

 Serial — AB-20, APP-182

METERS — See INSTRUMENTATION, CONTROLS

MIXERS — See also OSCILLATORS — AB-106, APP-135, APP-177

MODEMS — See also DEMODULATORS — APP-114

MODULATORS — See DEMODULATORS

MODULES, LOGIC (ENCAPSULATED) — See CIRCUITS

MSI — AB-55, AB-62, AB-76, AB-93, AB-97, AB-139, AB-142, AB-145, APP-160, APP-161, APP-163, APP-167, APP-169, APP-170, APP-173, APP-176, APP-178, APP-181, APP-182, TP-54

MULTICHANNEL ANALYZER — See INSTRUMENTATION, Nuclear

MULTIPLEXERS, DIGITAL — AB-63, AB-76, APP-181

MULTIPLIERS — AB-44, AB-50, APP-124

 Analog — AB-54, APP-164

 Digital — APP-163, APP-164, APP-172

MULTIVIBRATORS

 Astable — APP-143, TP-50

 Bistable — AB-23, AB-24, AB-33, AB-38, AB-64

 Monostable — APP-116, APP-173

N

NAVIGATION SYSTEMS

 Aircraft — APP-176, APP-178

 Radar — APP-76, APP-77, APP-81, APP-114

NOISE

 Immunity — APP-116, APP-166, TP-44, TP-46

 Low-Noise Techniques — AB-51, APP-105/4, APP-180

 Measurement — TP-44

 Pseudo-Random — AB-55

NUCLEAR ENVIRONMENT — See RADIATION EFFECTS ON SEMICONDUCTORS

O

ONE-SHOTS — See MULTIVIBRATORS, Monostable

OPTICAL

Describe Photo Device — AB-96

OSCILLATORS

Audio — AB-52, APP-103

Crystal-Controlled — AB-69, AB-99, APP-144, APP-145

Horizontal — APP-143, TP-50

Microwave — AB-59, APP-62

Multivibrator — See MULTIVIBRATORS

Pulse — APP-143

RF — APP-144, APP-156

Sinusoidal — AB-52, APP-124

Square-Wave — AB-99, APP-143, TP-50

Sweep — AB-68, APP-143, TP-50

Vertical — AB-68

Voltage-Controlled — AB-99, APP-143, TP-50

Wien Bridge — APP-103

P

PACKAGES, SEMICONDUCTOR

Aerospace and Defense — See PACKAGES, SEMICONDUCTOR, High Reliability, Severe Environment

Consumer and Commercial — See PACKAGES, SEMICONDUCTOR, Economy

High-Speed — See PACKAGES, SEMICONDUCTOR; High Reliability, Severe Environment

Materials — AB-6

Photo Devices — AB-70, APP-93

Severe Environment

High-g Loading — See Shock, Mechanical

Radiation Environments — AB-122

PACKAGING, SYSTEMS — AB-117

Interconnection Techniques

High-Speed — TP-46

Hybrid Circuits, — See also PACKAGING, SYSTEMS; Thick Film, Thin Film, — AB-16, AB-25

Interconnection Theory, Layout Rules & Hints — AB-6, APP-130, APP-131

Power (High Power) — AB-117

Printed Circuit Boards — Two Sided and Multilayer — AB-6, AB-16, AB-25, APP-130, APP-151

Soldering

General — AB-6

Wire Welding — AB-6

General Techniques — AB-6

PACKAGING, PHYSICAL PROTECTION

Severe Environment

High-g Loading — See Shock, Mechanical

Radiation Environments (Ionizing Radiation) — AB-122

Temperature, Extreme Temperature — AB-117

PAM, PCM, PDM, — See COMMUNICATION SYSTEMS

PARAMETER MEASUREMENT — TP-28, TP-40, TP-41

PARITY CHECKING GENERATION — APP-128, APP-131, APP-153, APP-163

PERIPHERAL EQUIPMENT — See COMPUTER

PHONOGRAPHS — See AMPLIFIERS, Audio; AMPLIFIERS, Hi-Fi

POWER SUPPLIES

General — APP-136

Converters — APP-88

Inverters — AB-30, AB-79

Regulators — AB-29, AB-60, AB-133, AB-146, APP-105/4, APP-116, APP-136, APP-149, APP-164, APP-165

PREAMPLIFIERS — See AMPLIFIERS

PRINTERS — See COMPUTER

PROGRAMMERS — See CONTROLS

R

RADAR — See also NAVIGATION SYSTEMS, Radar — APP-76

RADIATION EFFECTS ON SEMICONDUCTORS — TP-40, TP-41

RADIOS — See COMMUNICATION SYSTEMS

RATEMETER — See INSTRUMENTATION, Nuclear

READERS

Paper-Tape — AB-96

RECEIVERS — See COMMUNICATION SYSTEMS, COMPUTERS, NAVIGATION SYSTEMS

RECORDERS — See AMPLIFIERS, COMPUTER, CONTROLS, HIGH FIDELITY, INSTRUMENTATION,
MAGNETIC TAPE RECORDERS

RECTIFIERS — APP-105/4

Silicon-Controlled Rectifiers — AB-114

REGULATORS — See POWER SUPPLIES

RELAY DRIVERS, RELAYS — See also AMPLIFIERS — APP-166

REGISTER

Address — APP-172

Shift — AB-141, APP-131, APP-161, APP-182, APP-184

Multiple-Port — AB-97, APP-181

S

SCALERS, BINARY, DECADE — AB-23, AB-73, APP-181

SCANNERS — See DISPLAY

SENSORS — See also CONTROLS

Humidity — AB-112

Infra-red — AB-100

Light — AB-100, APP-93, APP-105/4

SERVO SYSTEMS — See CONTROLS — APP-87/1

SIMULATION, LOGIC — See LOGIC, Simulation

SOCKETS, INTEGRATED CIRCUITS — See PACKAGING

SPACE ENVIRONMENT — See RADIATION EFFECTS ON SEMICONDUCTORS

SUBSTRATES — See PACKAGING

SUBTRACTORS

Digital — APP-160, APP-163, APP-181

SWEEPS — See DEFLECTION

SWITCHES

Digital — AB-100

SYNTHESIZERS, FREQUENCY — See also COMMUNICATION SYSTEMS, INSTRUMENTATION — APP-176 APP-178, TP-52

T

TAPE READERS — See READERS

TAPE RECORDERS — See RECORDERS, MAGNETIC TAPE RECORDERS

TELEMETERING SYSTEMS — See COMMUNICATION SYSTEMS

TELEVISION — See also COMMUNICATION SYSTEMS

AGC Section — AB-80, TP-27, TP-47

Camera — AB-102, AB-103

Color Signal Processing Section — AB-69, AB-105, AB-124, AB-143, APP-145, TP-43, TP-48

Deflection Section — AB-68, APP-141, APP-143, TP-39

IF Section — AB-80, AB-95, AB-106, AB-118, AB-143, TP-35

Miscellaneous — APP-152

Receiver Systems — APP-149, APP-150, APP-174, TP-50, TP-52, SB-4

RF Section — AB-59, AB-81, APP-185, TP-36

Sound Section — APP-146, APP-158, APP-179, TP-42

Video Amplifier Section — AB-104, APP-67, TP-38

TERMINAL EQUIPMENT, DIGITAL — See PERIPHERAL EQUIPMENT

TEST EQUIPMENT — See INSTRUMENTATION

TESTERS — See INSTRUMENTATION

Function

DTL — AB-40

Discrete Device — AB-48

Linear — APP-125

TESTING — APP-112

THERMAL CONTROL — See CONTROL, PACKAGING

THRESHOLD DETECTORS — See DETECTORS

THYRISTER — AB-112, AB-113, AB-114, AB-116, TP-51

TIME BASE — See AMPLIFIERS, Deflection

TIMERS — AB-116, APP-61/2

TONE GENERATORS — See OSCILLATORS

TRANSCIVERS — See COMMUNICATION SYSTEMS

TRANSDUCERS — See also SENSORS — AB-51, APP-105/4

Diode — AB-70

TRANSMISSION SYSTEMS — See COMMUNICATION SYSTEMS

TRIGGERS — AB-114, AB-116, TP-51

TUNERS

All-Channel — TP-50

Television — APP-74, TP-50, TP-52

UHF — AB-59, AB-118, APP-185, TP-50

VHF — AB-118, APP-74, TP-50

V

VOLTAGE FOLLOWER — APP-105/4, APP-166

VOLTAGE REGULATOR — See POWER SUPPLIES, Regulation

W

WIDEBAND AMPLIFIERS — See AMPLIFIERS, Wideband

Y

Y PARAMETERS — APP-112

